

Date:

Exp No: 7

Name: Design a mod 4 Synchronous up/down counter with a control line using D flip flops.

Apparatus used:


1. D flip flops - 2
2. Xorgate - 1
3. clock

Theory:

UP/down counter is a combination of both up counter and down counter. It has a control line to select whether the counter is up counter or down counter.

& Since its Synchronous counter it has common clock for both flip flops.

State diagram:

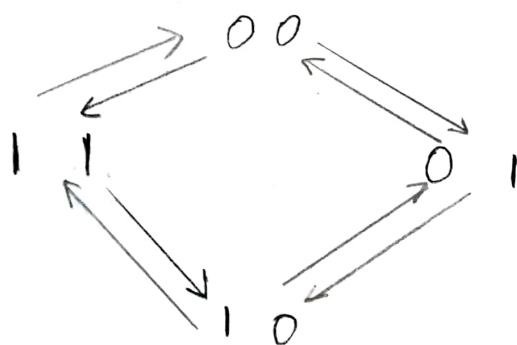

State table:

Ctrl I/p	Present state		Next state		Excitation table for Dff	
	Q_A	Q_B	Q_{An}	Q_{Bn}	D_A	D_B
0	0	0	0	1	0	1
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	0	0	0
1	1	0	0	1	0	1
1	1	1	1	0	1	0

K-maps:

1) D_A

C 0 1	$Q_A Q_B$			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$D_A = C \oplus Q_A \oplus Q_B$$

2)

C 0 1	$Q_A Q_B$			
	00	01	11	10
0	1	0	0	1
1	1	0	0	1

$$D_B = Q_B'$$

Practical Procedure:

- 1.) Ic's are placed on bread board
- 2.) connection are made as per designed circuit
- 3.) make sure of Power Supply is proper & adiquit