

Exp No: 12

Aim: Design 0-2-4-6 Self correcting to 0 Counter using D-flip flop.


Required:

- 1 - D-flip flop
- 2 - Connecting wires
- 3 - IC-Trainer Kit

Theory:

This kind of counter is used in counting numbers in given sequence. and once the sequence is complete it resets to 0.

State diagram:

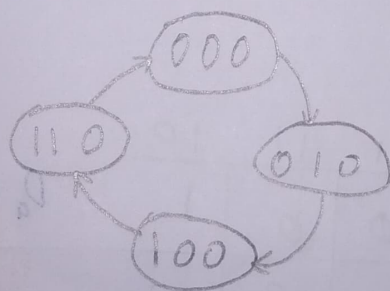

II Present state and next state table:

Excitation

PS			NS			Excitation		
q_a	q_b	q_c	Q_a	Q_b	Q_c	D_1	D_2	D_3
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	0
0	1	0	1	0	0	1	0	0
0	1	1	0	0	0	0	0	0
1	0	0	1	1	0	1	1	0
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0

Excitation table:

K map:

for D_1 :

q_c \ $q_a q_b$	00	01	11	10
0	0	0	0	1
1	0	0	0	0

$$D_a = q_c \bar{q}_a \bar{q}_b + \bar{q}_c q_a \bar{q}_b$$

$$\bar{q}_b (\bar{q}_a q_c + q_a \bar{q}_c)$$

for D_2


q_c \ $q_a q_b$	00	01	11	10
0	1	0	0	1
1	0	0	0	0

$$D_b = \bar{q}_c \bar{q}_a \bar{q}_b + \bar{q}_c q_a \bar{q}_b$$

$$= \bar{q}_c \bar{q}_b (q_a + \bar{q}_a)$$

$$\bar{q}_c \bar{q}_b$$

circuit for Counter:

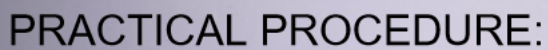

1. ICs are placed properly on the bread board of the IC trainer kit.
2. Connections are made as per the designed circuit diagram.
3. Power supply to the board is turned ON.
4. Circuit is verified as per the truth table of the circuit.

Student's observations:


1. it has 3 d-flip flops for showing pattern 0-2-4-6.
2. its used to count numbers in pattern required but for different pattern we use different circuit
3. all the flip flops has common clock so it is a synchronous counter.

Name:kaushik gupta


Date:13|4|21

regno:201900318


sign:kaushik

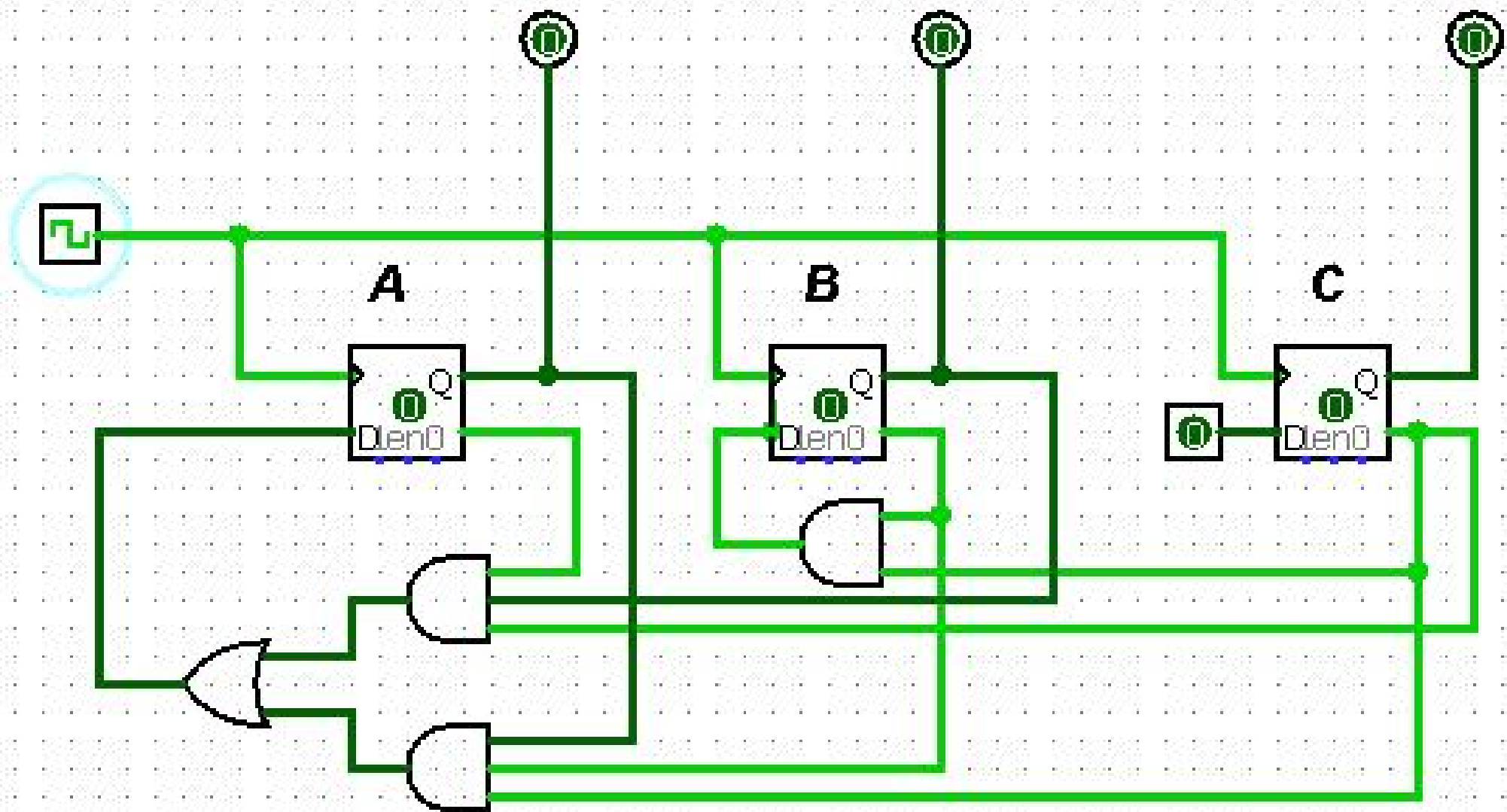


kaushik gupta 201900318

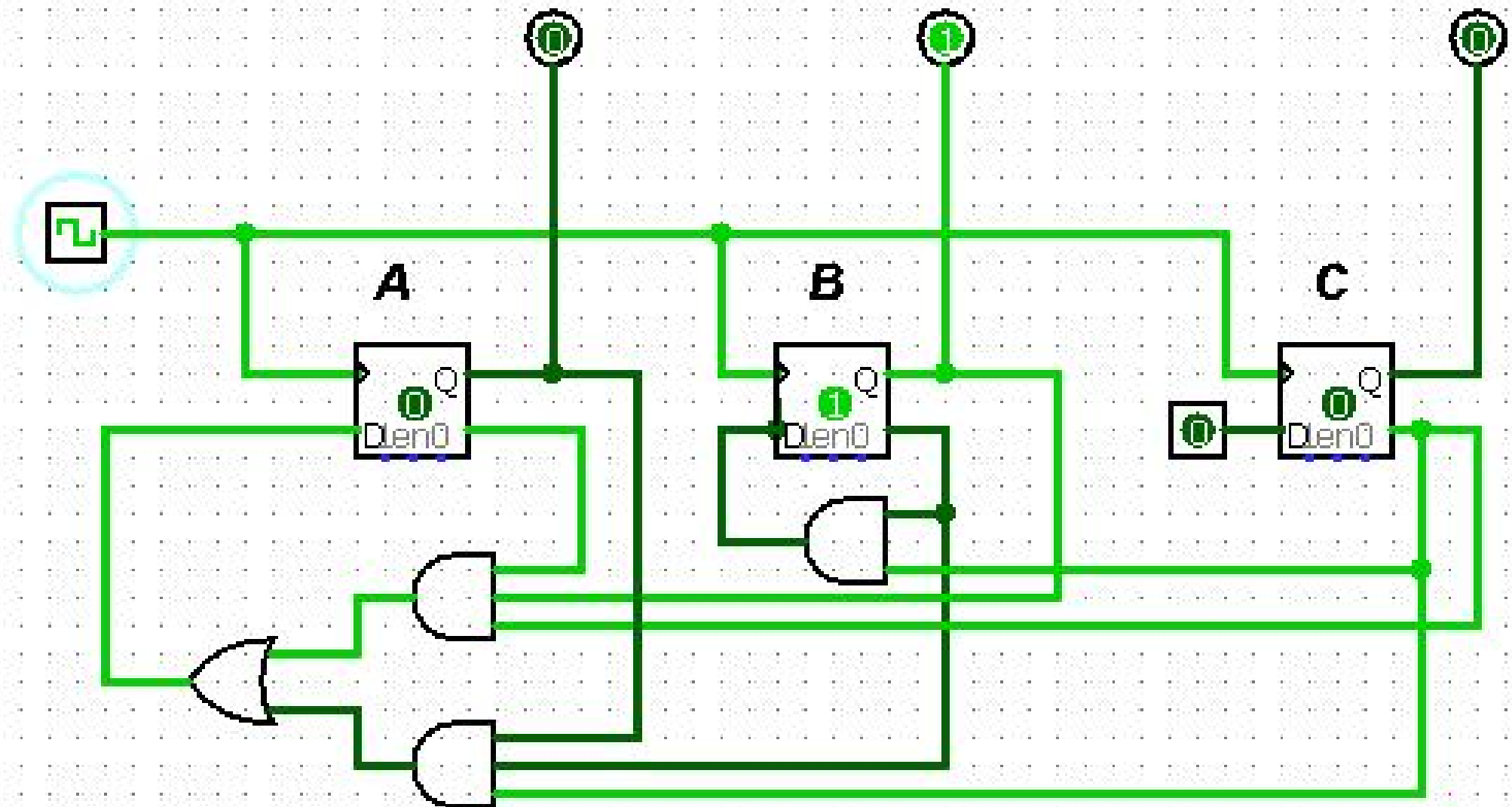

kaushik gupta 201900318

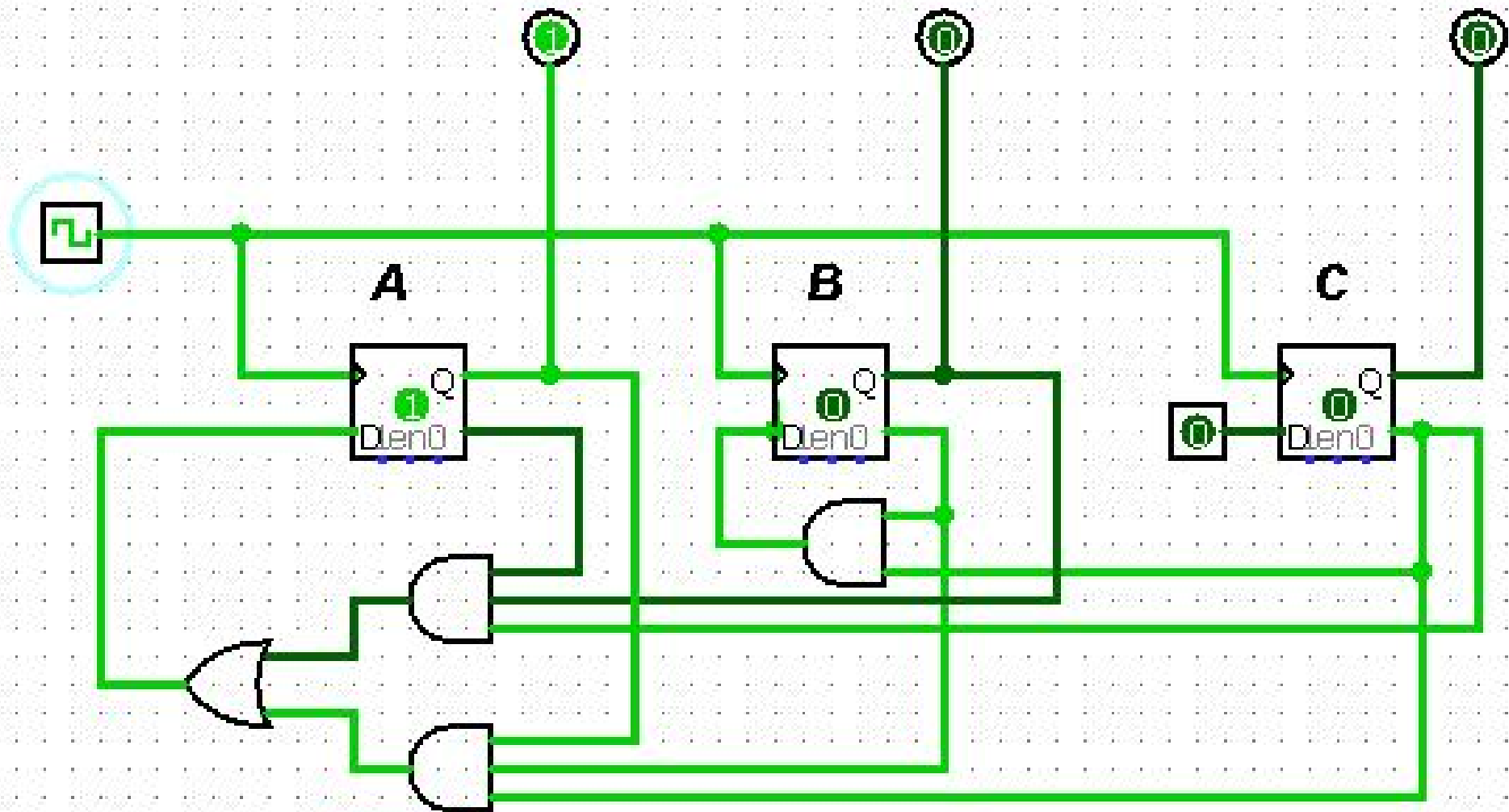

kaushik gupta 201900318

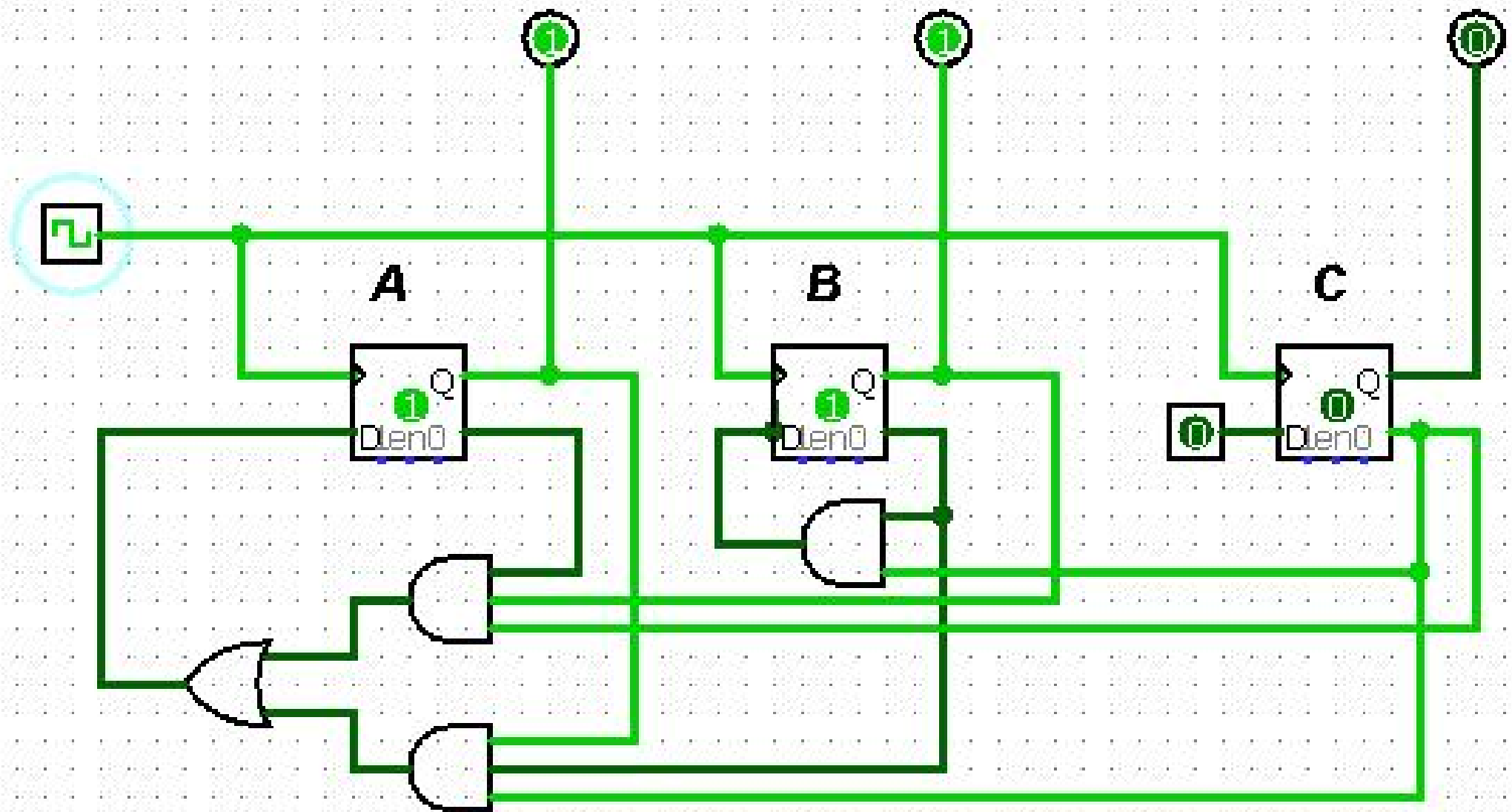

kaushik gupta 201900318